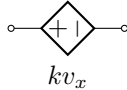


# Lecture 4, Jan 24, 2022


## Circuit Elements – Dependent Sources

- Linear dependent sources:

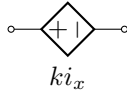
1. Voltage-dependent voltage source (controlled voltage source): voltage provided by the source is  $kv_x$  where  $v_x$  is the voltage somewhere in the circuit to which this source is connected
  - The voltage doesn't depend on the current that passes through; it depends on the voltage somewhere else in the circuit completely
  - Notation ( $v_x$  marked in the circuit):




- $k$  is dimensionless (voltage to voltage)
2. Current-dependent voltage source: voltage provided is  $ki_x$ , like the voltage-dependent voltage source but for current
  - Notation ( $i_x$  marked in the circuit):



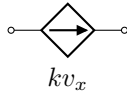- $k$  has dimensions of voltage over current, V/A
3. Voltage-dependent current source: current output is  $kv_x$ 
  - Notation ( $v_x$  marked in the circuit):



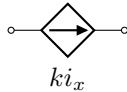- $k$  has dimensions of current over voltage, A/V
4. Current-dependent current source: current output is  $ki_x$ 
  - Notation ( $i_x$  marked in the circuit):




- $k$  is dimensionless (current to current)
- Just like independent sources, perfectly linear dependent sources don't exist in the real world, but under certain conditions we can use them to model real things

## Other Circuit Elements

- Resistors: ratio of voltage over current is always a constant,  $\frac{v}{i} = R$

- Notation:

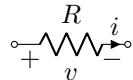

- The relation  $\frac{v}{i} = R$  is only true when PSC holds (when it doesn't, we need a minus sign)
- $R$  has units of  $A/V = \Omega$  (Ohm)
- Alternatively,  $G = \frac{1}{R}$  is the *conductance* (as opposed to  $R$  being the *resistance*), which has units of  $\Omega^{-1} = \text{S}$  (mho) or Siemens Si
- Assuming  $R$  is positive, power going through will always be positive, i.e. the resistor always consumes power